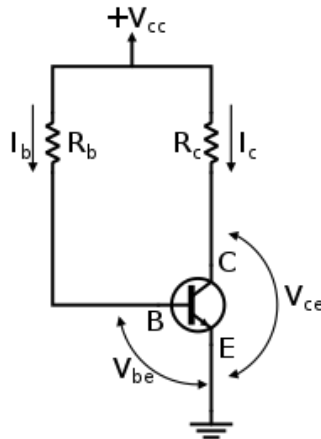



Assignment-02 Basic Electronics

Full marks-05

1. The BJT circuit shown below, given $V_{CC}=22V$, $R_b=2.2M\Omega$, $R_c=10K\Omega$. If the BJT is a Silicon BJT with $\alpha=0.98$, then find (I) I_B (II) I_C , (III) V_{CE} (IV) V_{CB} .



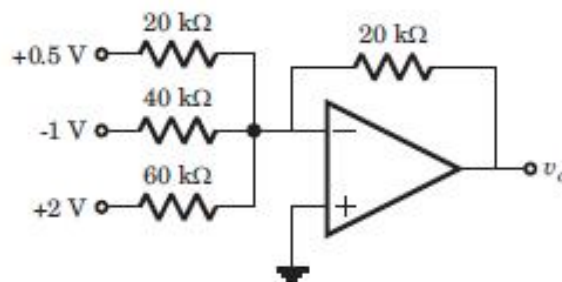2. Design a summing amplifier to get $V_0 = -V_1 + 2V_2 - 5V_3$. Explain your design strategy in details with diagram. Note that only V_1 , V_2 and V_3 are the prime inputs.
3. Estimate the output voltage of the OPAMP circuit shown below:



4. Convert the following codes (with derivation) as instructed. Sub-scripted number indicates base of the number.:

- A. $(51.835)_{10} = (?)_2$
- B. $(DE.3CA)_{16} = (?)_2$
- C. $(743.326)_8 = (?)_{16}$
- D. $(87.334)_{10} = (?)_8$